

B.E.(with Credits)-Regular-Semester 2012-Electronics & Telecommunication / Communication  
Engineering / Electronics Engineering Sem V  
**ET/EN/EC501 - Linear Electronic Circuits / Linear Integrated Circuits**

P. Pages : 2

Time : Three Hours



**GUG/S/18/3744**


Max. Marks : 80

- Notes :
1. All questions carry marks as indicated.
  2. Due credit will be given to neatness and adequate dimensions.
  3. Assume suitable data wherever necessary.

1. a) The differential amplifier uses a transistor which has  $\beta = 200$  and it is biased at  $I_{CQ} = 100\mu A$ . Determine  $R_C$  and  $R_E$  so that  $A_{dm} = 500$  and  $CMRR = 80dB$ . **8**
- b) What is common mode Rejection Ratio? Why it is very very high? **8**

**OR**

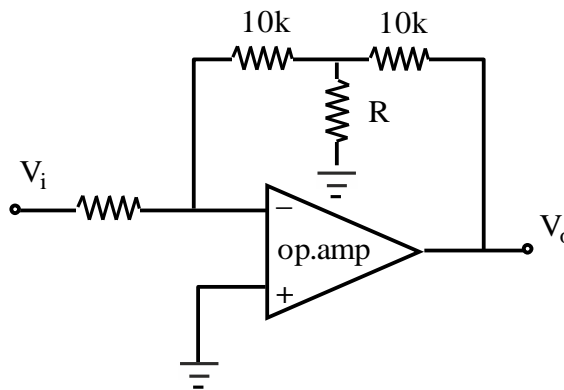2. a) For an inverting amplifier following data are given. **10**  
 $A = 2 \times 10^5$ ,  $R_i = 2m\Omega$ ,  $R_o = 75\Omega$ ,  $U_{GB} = 1MHz$ , supply voltage =  $\pm 15V$ . Maximum output voltage swing =  $\pm 13V$   $R_1 = 1.8k$ ,  $R_f = 18k$ , compute the closed loop parameter  $A_f$ ,  $A_{if}$ ,  $R_{of}$  and  $F_t$ ,  $V_{oot}$ , if  $v_{in} = 1$  volt peak to peak sine wave at  $100Hz$ .  
i) Compute output voltage  $V_o$ .  
ii) Draw the output waveform.
- b) Explain the purpose of constant current source in differential amplifier. **6**
3. a) For the circuit shown, calculate the value of 'R' required to obtained  $V_o = -50V_i$ . **8**



- b) Draw and explain grounded load voltage to current converter. **8**

**OR**

4. a) What are the limitations of ideal integrator circuit? How can be they eliminated in practical ore? **8**

- b) The op-amp used as non-inverting amplifier has following specification. 8

$$\frac{\Delta V_{ios}}{\Delta T} = 30 \mu\text{V}/^{\circ}\text{C}, \quad \frac{\Delta I_{ios}}{\Delta T} = 10 \text{ nA}/^{\circ}\text{C}$$

The amplifier is nulled at 25°C and uses  $R_1 = 100\Omega$  and  $R_f = 8.2\text{k}\Omega$ . If a 20mv peak to peak sine wave at 1000Hz is applied as input, calculate error voltage and output voltage at 45°C.


5. a) Explain the full-wave precision Rectifier using op-amp with the help of waveform and derivation. 8

- b) Draw and explain the working of IC741 as a stable multivibrator and write the equation for its frequency of oscillation. 8

**OR**

6. a) Draw and explain analog multiplier circuit using op-amp. 8

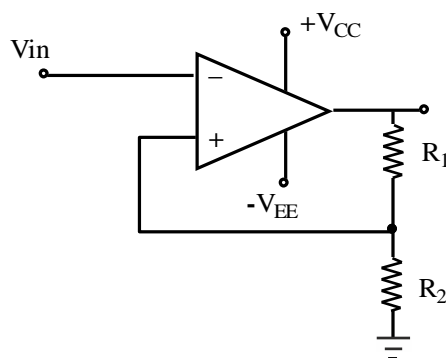- b) For the regenerative comparator shown in figure, determine the threshold voltages, Hysteresis voltage and draw the Hysteresis curve. Assume op-amp with saturation voltage = 12V,  $R_1 = 2\text{k}\Omega$ ,  $R_2 = 3\text{k}\Omega$  and  $V_{\text{ref}} = -4\text{V}$ . 8



7. a) Design a 2<sup>nd</sup> order Butterworth low pass filter whose bandwidth is 1.5KHz use all capacitor of 100nf. 8

- b) Draw and explain sample and Hold circuit with waveform. 8

**OR**

8. a) What is oscillator? Explain Wein bridge oscillator in detail. 8

- b) Draw and explain in detail the working of successive approximation type A to D converter. 8

9. a) Draw and explain the working of mono stable multivibrator using the IC555 and show the pulse width  $T = 1.1 RC$ . 8

- b) Draw the basic building block of PLL. Also define capture range and lock range. 8

**OR**

10. a) Draw block diagram of IC723 voltage regulator and explain working of each block. 8

- b) Design a square wave generator using IC555 having output frequency 15KHz and Duty cycle 60%. 8

\*\*\*\*\*