

B.E. Instrumentation Engineering (C.B.C.S. Pattern) Sem-III
3BEIE03 - Network Theory

P. Pages : 4

Time : Three Hours



GUG/S/19/11513

Max. Marks : 80

- Notes :
1. All questions carry marks as indicated.
 2. Due credit will be given to neatness and adequate dimensions.
 3. Assume suitable data wherever necessary.

1. a) Find the value of R_1 & R_2 in the network shown in figure 1, using mesh analysis. **8**

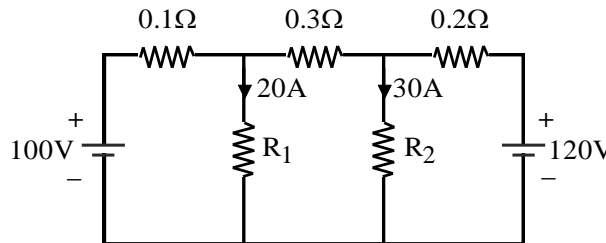


Figure 1

- b) Find out the voltage across 40Ω and the power supplied by the $5A$ source using nodal analysis for the network shown in figure 2. **8**

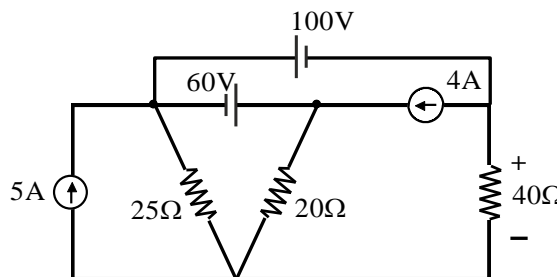


Figure 2

OR

2. a) Find out the power delivered to the 4Ω resistor using mesh analysis for the network shown in figure 3. To what voltage should the $100V$ battery be changed so that no power is delivered to the 4Ω resistor ? **8**

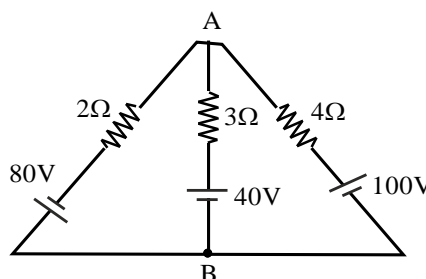


Figure 3

- b) Write a short note on :
- i) Supermesh
 - ii) Supernode

8

3. a) State and discuss reciprocity theorem. 8
- b) Find the Thevenins and Norton's equivalents for the circuit shown in figure 4 with respect to terminal ab. 8

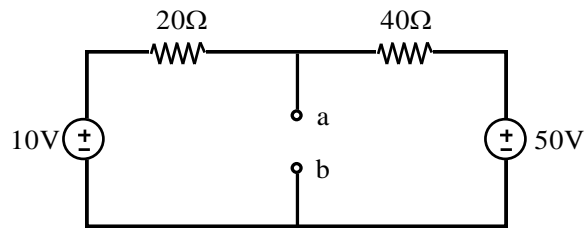


Figure 4

OR

4. a) State the maximum power transfer theorem for the d.c. circuits. Also derive the condition for maximum power transfer. 8
- b) Calculate the current I in the network shown in figure 5, using Millman's theorem. 8

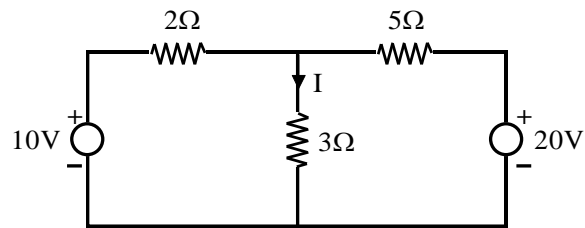


Figure 5

5. a) Obtain the expression for the complex impedance for the ckt shown in the figure 6. Also draw impedance diagram. 8

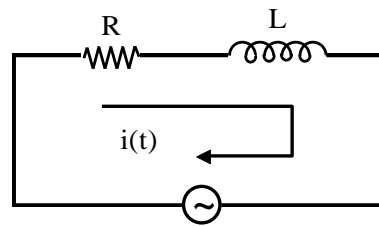


Figure 6

- b) For the circuit shown in figure 7, a voltage $V(t)$ is applied in the resulting current in the circuit $i(t) = 15 \sin(\omega t + 30^\circ)$ A. Determine the active power, reactive power, power factor & the apparent power. 8

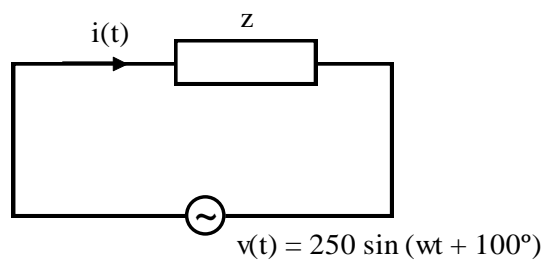


Figure 7

OR

6. a) Determine the equivalent impedance of the network shown in figure. 8. 8

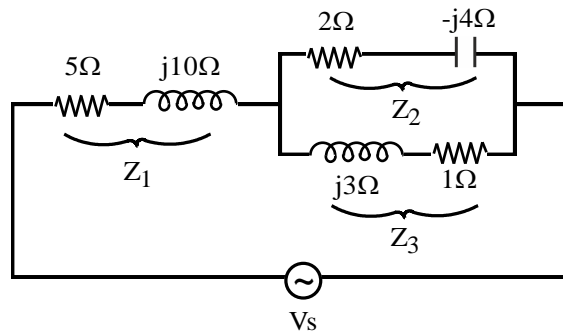


Figure 8

- b) Two impedances, $z_1 = 10 \angle -60^\circ \Omega$ & $z_2 = 16 \angle 70^\circ \Omega$ are in series and pass an effective current of 5A. Determine the active power, reactive power, apparent power and power factor. 8

7. a) Determine the Thevenin's equivalent between the output terminals for the network shown in figure 9. 8

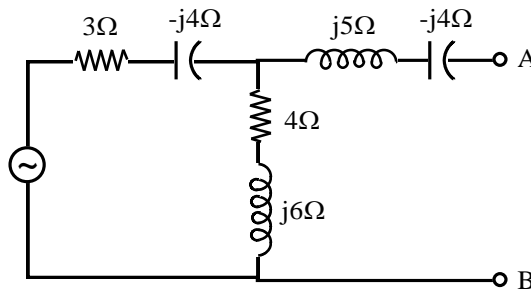


Figure 9

- b) In the network shown in figure 10, the switch is moved from position 1 to position 2 at $t=0$. The switch is in position 1 for a long time. Determine the current expression $i(t)$. 8

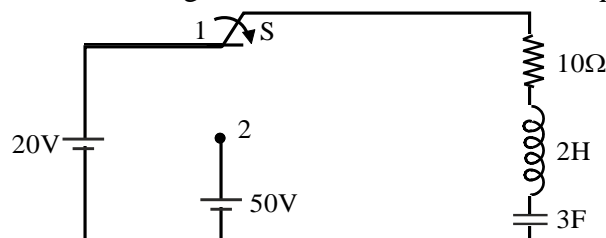


Figure 10

OR

8. a) In the circuit shown in figure 11, determine the current equations for i_1 and i_2 when the switch is closed at $t = 0$. 8

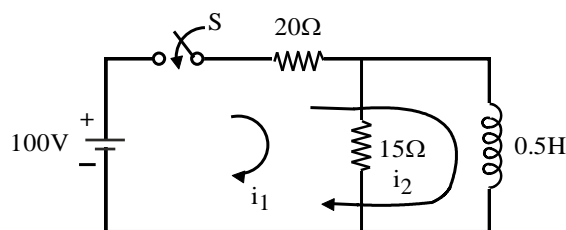


Figure 11

- b) For the circuit shown in figure 12, find the value of z that will receive maximum power. Also determine this power. 8

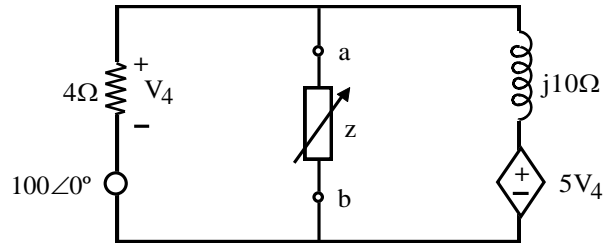


Figure 12

9. a) Find the Y-parameter for the network shown in figure 13. 8

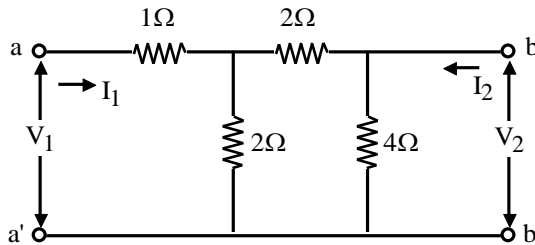


Figure 13

- b) Define z-parameters for two port network. Also express the z parameters in terms of Y-parameters. 8

OR

10. a) Find the h-parameters of the network shown in figure 14. 8

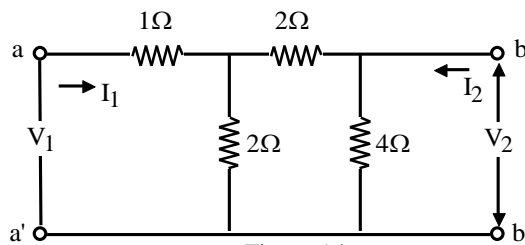


Figure 14

- b) Define two-port networks discuss the open circuit impedance (z) parameters and short circuit admittance (Y) parameters. 8
