

Bachelor of Science (S.Y. B.Sc.) Third Semester
B.Sc.23132 - Electronics Paper-II (Digital Electronics-I)

P. Pages : 1

Time : Three Hours



GUG/W/18/1263

Max. Marks : 50

- Notes : 1. All questions are compulsory and carry equal marks.
2. Draw neat and well labelled diagram wherever necessary.

1. Either

- a) Explain SOP and POS form with suitable example.
Minimize the four variable logic function using K-map. **6+4**
 $f(A, B, C, D) = \sum m(1,3,7,11,15) + d(0,2,5)$

OR

- b) Draw the logic diagram of 1:4 MUX using logic gate and explain its working with truth table.
Obtain 8:1 MUX using 4:1 MUX and explain it with truth table. **5+5**

2. Either

- a) Explain the concept of decoder. Draw the block diagram of BCD to seven segment decoder using IC 7447 and explain it with truth table. **3+7**

OR

- b) Explain half adder and full adder with logic diagram and truth table. What is 4 bit binary adder? Draw 4 bit binary adder diagram using IC 7483. **7+3**

3. Either

- a) What is flip flop? Draw R-S flip flop using NAND gate and explain its working.
Explain the working of DFF with suitable diagram. State any two applications of it. **5+5**

OR

- b) Draw the logic diagram of JKFF and explain its working with truth table.
What is race around condition? How can it be removed? **6+4**

4. Either

- a) Explain the construction and working of 4 bit ripple counter. Draw its timing diagrams.
Differentiate between synchronous and asynchronous counter. **6+4**

OR

- b) What is modulus of a counter? Explain the construction and working of MOD 5 counter.
Explain the working of 4 bit ring counter with timing diagram. **6+4**

5.

- a) Draw logic diagram of 1:4 DEMUX using logic gate and explain it.
b) Explain the concept of encoder.
c) Explain the function of preset and clear inputs of FF.
d) Explain Johnson counter. **2^{1/2}x4**
