

M.Sc. (Physics) (C.B.C.S. Pattern) Sem-III  
**PSCPHYT11-4-Paper-XI : (Core Elective-E1.4) : Applied Electronics-I**  
**(PSCPHYT.11)**

P. Pages : 2

Time : Three Hours



**GUG/S/19/11301**

Max. Marks : 80

---

**1.** Either

- a) Discuss Op-Amp with Block diagram. Explain the use of operational amplifier as integrator and differentiator. **10**
- b) Explain scaling and averaging amplifier. **6**

**OR**

- e) Explain construction and working of phase shift oscillator and LC tunable oscillator. **8**
- f) Explain monostable and astable multivibrators with their time diagrams. **8**

**2.** Either

- a) What are modulation and demodulation? Discuss amplitude modulation and generation of AM-waves. **8**
- b) What is DSBSC modulation? Discuss the generation and coherent detection of DSBSC waves. **8**

**OR**

- e) Discuss Fresnel zone problem and ground reflection with respect to microwave communication. **8**
- f) Explain the atmospheric effect on the propagation of waves. Discuss the use of antennas in microwave communication system. **8**

**3.** Either

- a) Discuss IC-8085 microprocessor with Pin diagram. **8**
- b) Discuss D/A converters. Explain ladder and weighted register type D/A converter. **8**

**OR**

- e) Discuss demultiplexer. Explain the working of 1:4 demultiplexer with suitable diagram. **8**
- f) Explain assembly language programmes. **8**

- 4. Either**
- a) Explain the reflex 'Klystrons' used as microwave device. Discuss principle of two cavity Klystrons and reflex Klystrons. **8**
  - b) What are wave modes? Explain the working of Helix travelling wave tubes for the generation of microwaves. **8**

**OR**

- e) Discuss velocity modulation used in microwave generation. **8**
- f) Write short note on: **8**
  - i) Read diode
  - ii) IMPATT diode

- 5. All questions are compulsory.**
- a) Explain CMRR in Op-Amp. **4**
  - b) Discuss frequency division multiplexing. **4**
  - c) Explain stack and sub routings. **4**
  - d) Explain basic principle of two cavity Klystrons. **4**

\*\*\*\*\*